

All India Mock GATE Test Series
Test series 4
Electronics & Communication Engineering

Answer Keys and Explanations


General Aptitude:

1. **[Ans. A]**
Meaning: slow to move or act
Part of Speech: Adjective

2. **[Ans. *] Range: 9 to 9**
Clearly $5 \times 2 = 10, 10 \times 2 = 20, 20 \times 2 = 40, \dots$
So, the series is a G.P. in which $a_1 = 5$ and $r = 2$
To find the n^{th} term of a Geometric progression, the formula is $a_n = a_1 r^{n-1}$
Let 1280 be the n^{th} term of the series
Then, $5 \times 2^{n-1} = 1280 \Leftrightarrow 2^{n-1} = 256 = 2^8 \Leftrightarrow n - 1 = 8 \Leftrightarrow n = 9$


3. **[Ans. A]**
For this type of question take the LCM of speeds and assume the LCM as the distance
Then the time taken at speed of 60 km/hr = $\frac{300}{60} = 5$ hrs
Again the time taken at speed of 50 km/hr = $\frac{300}{50} = 6$ hrs
Thus we see that in place of 5 hrs trains take 6 hrs. Its means train takes 1 hr extra and this one hour is stopping period in the total time of 6 hrs. Thus in 6 hrs train halts for 1 hr. so in 1 hr train will stop for $\frac{1}{6}$ hours or 10 minutes.

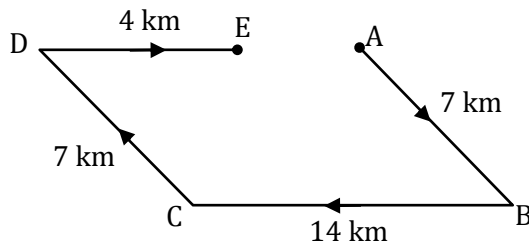4. **[Ans. *] Range: 10 to 10**
Let assume, Radha is at Point 'A'



Required distance = $AE = AD - DE$
Since ABCD is a parallelogram
 $AD = BC$
 $\therefore AE = BC - DE$
 $= 14 - 4 = 10$

5. [Ans. A]

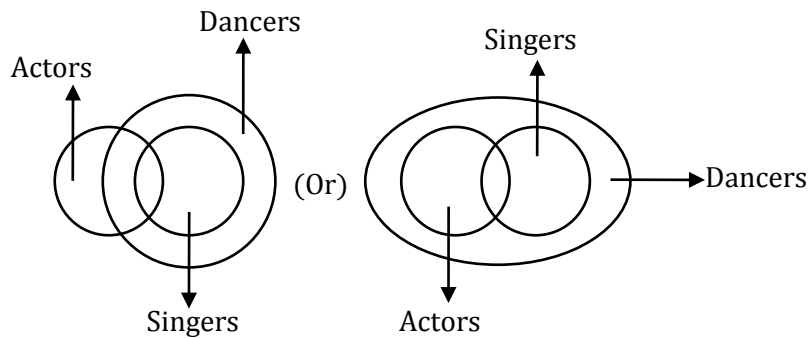

Only (1) Follows

6. [Ans. *] Range: 6 to 6

Given:

$$\begin{array}{l}
 R \rightarrow x + 10 \\
 L \rightarrow x + 6 \\
 B \rightarrow x + 5 \\
 H \rightarrow x + 4 \\
 A \rightarrow x
 \end{array}
 \left. \begin{array}{l}
 x \\
 x \\
 x + \\
 x \\
 x
 \end{array} \right\}
 \begin{array}{l}
 x + 5 \\
 x + 5 \\
 x + 5 \\
 x + 5 \\
 x + 5
 \end{array}
 \left. \begin{array}{l}
 \textcircled{5}^+ \\
 \textcircled{1}^+ \\
 \textcircled{1}^- \\
 \textcircled{5}^-
 \end{array} \right\}$$

Thus total 6 coins have to be transferred.

7. [Ans. B]

The numbers are given in pair of 4 and 9.

The unit digit of each pair is 4, and there are 50 such pairs which are mutually multiplied together.

$$\text{Unit digit } \underbrace{4 \times 9^2}_4 \times \underbrace{4^3 \times 9^4}_4 \times \underbrace{4^5 \times 9^6}_4 \times \dots \underbrace{4^{99} \times 9^{100}}_4$$

Again $4 \times 4 \times 4 \times 4 \dots 4$ (upto 50 times)

i.e., the unit digit of 4^{50} , which is 6

[Since unit digit of 4^{2n} is 6 for $n = 1, 2, 3, \dots$ etc]

8. [Ans. B]

$$\begin{array}{ccc}
 16.66 & & 18.75 \\
 & \diagdown & / \\
 & 17.5 & \\
 & / & \diagdown \\
 \text{(Boys)} & & \text{(Girls)}
 \end{array}$$

$$\Rightarrow \begin{array}{ccc}
 \frac{50}{3} \times \frac{4}{4} & & \frac{75}{4} \times \frac{3}{3} \\
 & \diagdown & / \\
 & \frac{35}{2} \times \frac{6}{6} & \\
 & / & \diagdown \\
 B & & G
 \end{array} \quad \dots \dots \text{(Making Denominator equal)}$$

$$\Rightarrow \begin{array}{ccc}
 200/12 & & 225/12 \\
 & \diagdown & / \\
 & 210/12 & \\
 & / & \diagdown \\
 15/12 & & 10/12 \\
 \Rightarrow & 3 & : \quad 2
 \end{array}$$

∴ Boys = 3x; Girls = 2x

Given 3x – 2x = 8

∴ x = 8

Thus the number of Girls = 16 and number of Boys = 24

9. [Ans. D]

Let there be x voters and k votes goes to loser then

$0.8x - 120 = k + (k + 200) \dots \dots \textcircled{1}$

Also, $k + 200 = 0.41x \dots \dots \textcircled{2}$

From equation $\textcircled{1}$ and $\textcircled{2}$

$0.8x - 120 = 0.41x - 200 + 0.41x$

$0.02x = 80$

$x = 4000$

∴ $k = 0.41 \times 4000 - 200$

$\Rightarrow k = 1440$

And $(k + 200) = 1640$

Number of voters voted = $x - 0.2x$

$0.8x = 0.8 \times 4000 = 3200$

Therefore, percentage of votes for defeated candidates = $\frac{1440}{3200} \times 100 = 45\%$

10. [Ans. *] Range: 40 to 40

Given

$W_2 = 1.5 W_1$... (50% Increase in work)

$D_1 = D_2$

$$\therefore \frac{M_1 \times D_1}{W_1} = \frac{M_2 \times D_2}{W_2}$$

$$\therefore M_2 = 1.5 M_1$$

\therefore If the efficiency of M_1 and M_2 is same, then 50% more work force is required.

But it is given the productivity of new labour is 25% more (i.e., 5/4 times efficient)

$$\therefore \text{Actual \% increase in work force required} = \frac{50\%}{5/4} = 40\%$$

Technical:

1. **[Ans. B]**

Writing characteristics equation for A

$$\begin{bmatrix} a-\lambda & 1 & 0 & 0 \\ 1 & a-\lambda & 0 & 0 \\ 0 & 0 & 1-\lambda & -1 \\ 0 & 0 & -1 & 1-\lambda \end{bmatrix} = (a-\lambda) \left((a-\lambda) \begin{vmatrix} 1-\lambda & -1 \\ -1 & 1-\lambda \end{vmatrix} \right) - 1 \left(1 \cdot \begin{vmatrix} 1-\lambda & -1 \\ -1 & 1-\lambda \end{vmatrix} \right)$$

$$= ((a-\lambda)^2 - 1) \begin{vmatrix} 1-\lambda & -1 \\ -1 & 1-\lambda \end{vmatrix} ((a-\lambda)^2 - 1)(\lambda^2 - 2\lambda) = 0$$

Which can be expressed as?

$$(a - \lambda^2) - 1 = 0 \text{ or } \Rightarrow (a - \lambda) = \pm 1$$

$$(\lambda^2 - 2\lambda) = 0 \Rightarrow \lambda = a + 1, \lambda = a - 1$$

$$\Rightarrow \lambda(\lambda - 2) = 0$$

$$\lambda = 0, \lambda = 2$$

$$\text{So, } \lambda = a + 1, \lambda = a - 1, \lambda = 0, \lambda = 2$$

Alternative Method:

$$\text{Sum of Eigen values} = 2a + 2$$

Only (B) satisfies

2. **[Ans. A]**

$$\oint_c \frac{f(z)}{(z - z_0)^{n+1}} dz = 2\pi i \frac{f^n(z_0)}{n!}$$

$$= 2\pi i \frac{81 \cos h(0)}{4!}$$

$$= \frac{27}{4} \pi i$$

3. **[Ans. *] Range: 2 to 2**

$$\text{Rank}(A^T A) = \text{rank}(A)$$

$$\begin{pmatrix} 1 & 3 & 1 & -4 \\ -1 & -3 & 1 & 0 \\ 2 & 6 & 2 & -8 \end{pmatrix} \begin{matrix} R_2 \rightarrow R_2 + R_1 \\ R_3 \rightarrow R_3 - 2R_1 \end{matrix}$$

$$\begin{pmatrix} 1 & 3 & 1 & -4 \\ 0 & 0 & 2 & -4 \\ 0 & 0 & 0 & 0 \end{pmatrix}$$

$$\text{Rank}(A) = 2$$

$$\therefore \text{Rank}(A^T A) = 2$$

4. [Ans. *] Range: 9 to 9

The curve intersects the x-axis at $x = 1$

$$((x - 1)^{1/3} = 0 \Rightarrow x = 1)$$

Given

$$\int_1^k (x - 1)^{1/3} dx = 12$$

$$\left. \frac{(x - 1)^{4/3}}{\frac{4}{3}} \right|_1^k = 12$$

$$\frac{(k - 1)^{4/3}}{\frac{4}{3}} - 0 = 12$$


$$\Rightarrow k = 9$$

5. [Ans. D]

The direction of steepest ascent of $z(x, y)$ is given by $\nabla z|_{\text{at } P(3,-6)}$

$$\begin{aligned} \nabla z &= i \frac{\partial z}{\partial x} + j \frac{\partial z}{\partial y} \\ &= -8xi - 2yj |_{(3,-6)} \\ &= -24i + 12j \end{aligned}$$

6. [Ans. C]

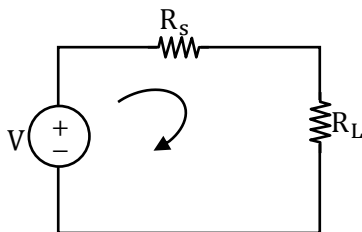


$$P_L = i_L^2 \times R_L$$

$$P_L = \left(\frac{V}{R_s + R_L} \right)^2 R_L$$

$$P_{L_{\max}} = \frac{V^2}{4R_L} \text{ at } R_L = R_s \leftarrow \text{maximum power transfer theorem}$$

When $R_L = 0$, $P_L = 0$

$R_L = \infty$, $i_L = 0$ so $P_L = 0$

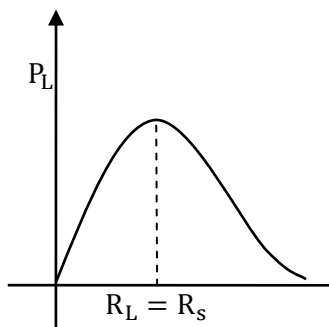

7. [Ans. *]Range: 4.20 to 4.50

For first order RC Circuit

$$V_C(t) = V_C(\infty) - [V_C(\infty) - V_C(0^+)]e^{-t/RC}$$

$$i_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$i_C(t) = \frac{1}{RC} [V_C(\infty) - V_C(0^+)]e^{-t/RC}$$

$$i_C(0) = \frac{1}{RC} [V_C(\infty) - V_C(0^+)] = 5A$$


At $t=3ms$

$$i(t) = 2.5 = 5e^{-3m/RC}$$

$$\frac{1}{2} = e^{-\frac{3m}{C}}; R = 1$$

$$C = \left[\frac{3m}{\ln(2)} \right] = 4.328mF$$

8. [Ans. B]

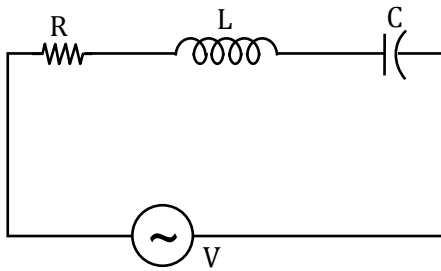

$$Z = R + j\omega L - \frac{j}{\omega C}$$

$$Y = \frac{1}{R + j(\omega L - 1/\omega C)}$$


$$= \frac{1}{\omega C} > \omega L [\text{at lower frequency}]$$

$$\text{So, } Y = \frac{1}{R - jX} \quad |X| = [\omega L - 1/\omega C]$$

$$Y = \frac{R + jX}{R^2 + X^2} \rightarrow \text{Inductive load}$$

9. [Ans. B]

Convert inner delta into star:

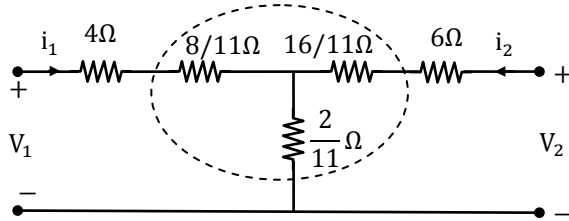

By applying KVL in both side

$$V_1 = \left(4 + \frac{10}{11}\right) i_1 + \frac{2}{11} i_2 \dots\dots \textcircled{1}$$

$$V_2 = \frac{2}{11} i_1 + \left(6 + \frac{18}{11}\right) i_2 \dots\dots \textcircled{2}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0}$$

By equation $\textcircled{2}$

$$-\frac{2}{11} i_1 = \frac{66 + 18}{11} i_2$$

$$\frac{i_1}{i_2} = -\frac{84}{2} = -42; \frac{i_2}{i_1} = \frac{-1}{42}$$

10. [Ans. *] Range: 9.3 to 9.5

$$H(\omega) = 9 \int_{-\infty}^{\infty} \left| \frac{\sin\left(\frac{\omega}{3}\right)}{\omega} \right|^2 d\omega$$

Let,


$$x(\omega) = \left(\frac{\sin\left(\frac{\omega}{3}\right)}{\left(\frac{\omega}{3}\right)} \right) = \text{Sa} \left[\frac{\omega}{3} \right]$$

$$x^2(\omega) = \left(\frac{\sin\left(\frac{\omega}{3}\right)}{\left(\frac{\omega}{3}\right)} \right)^2 = \text{Sa}^2 \left[\frac{\omega}{3} \right]$$

$$H(\omega) = 1 \int_{-\infty}^{\infty} \text{Sa}^2 \left[\frac{\omega}{3} \right] \cdot d\omega$$

Parseval's Theorem:

$$\int_{-\infty}^{\infty} |x(t)|^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |x(\omega)|^2 d\omega$$

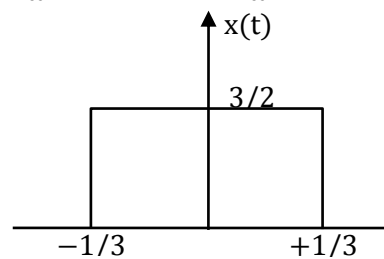

$$\begin{aligned} \text{F.T} \\ \leftrightarrow \quad |x(\omega) &= \text{Sa} \left(\frac{\omega}{3} \right) \\ A\tau &= 1 \\ \tau/2 &= 1/3 \\ \tau &= 2/3 \end{aligned}$$

$$\Rightarrow \int_{-\infty}^{\infty} \text{Sa}^2 \left(\frac{\omega}{3} \right) \cdot d\omega = 2\pi \int_{-\infty}^{\infty} (x(t))^2 dt$$

$$= 2\pi \int_{-1/3}^{+1/3} \left(\frac{3}{2} \right)^2 dt \Rightarrow 2\pi \frac{9}{4} [t]_{-1/3}^{+1/3}$$

$$\Rightarrow 2\pi \times \frac{9}{4} \times \left[\frac{2}{3} \right]$$

$$\Rightarrow 3\pi = 9.42$$

11. [Ans. A]

12. [Ans. *] Range: 1.210 to 1.215

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_t)^2 \text{ [When no - channel length modulation involved]}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) [V_{gs} - V_t]^2 (1 + \lambda V_{DS}) \text{ Where } \lambda \text{ is channel length modulation}$$

$$I_{D(\text{sat})} = 1.2 \text{ mA (Without } \lambda)$$

$$I_D = 1.2 (1 + 0.002 \times 5) = 1.212 \text{ mA}$$

13. [Ans.*]Range: 79 to 81


$$I_{\text{knee}} + I_R = \frac{10 - 6}{50} = \frac{4}{50} = 80\text{mA}$$

$$I_R = 80\text{mA} - I_{\text{knee}} = 80 - 5 = 75\text{mA}$$

$$\text{Now } I_R \times R = 6$$

$$\Rightarrow R = \frac{6}{75\text{mA}} = 80\Omega$$

14. [Ans. A]

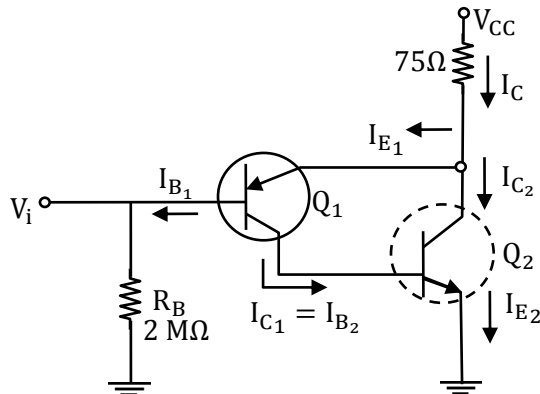

$$I_{E1} + I_{C2} = I_C$$

$$\approx I_{C1} + I_{C2}$$

$$= I_{B2} + I_{C2}$$

$$\approx I_{C2}$$

$$\therefore V_{CC} - I_C R_C - V_{E_{B1}} - I_{B1} R_B = 0$$

$$\Rightarrow V_{CC} - I_{C2} R_C - V_{E_{B1}} - I_{B1} R_B = 0$$

$$\Rightarrow V_{CC} - \beta_2 I_{B2} R_C - V_{E_{B1}} - I_{B1} R_B = 0$$

$$\Rightarrow V_{CC} - \beta_2 I_{C1} R_C - V_{E_{B1}} - I_{B1} R_B = 0$$

$$\Rightarrow V_{CC} - \beta_1 \beta_2 I_{B1} R_C - V_{E_{B1}} - I_{B1} R_B = 0$$

$$\Rightarrow I_{B1} = \frac{V_{CC} - V_{E_{B1}}}{R_B + \beta_1 \beta_2 R_C}$$

$$= \frac{17.3}{2\text{M}\Omega + (140)(180)(75)}$$

$$= \frac{17.3}{3.89 \times 10^6} = 4.45 \mu\text{A}$$

15. [Ans. C]

$$I_E = \frac{4\text{V} - 0.7}{3.3\text{k}} = 1\text{mA}$$

$$\therefore r_e = \frac{26\text{mV}}{1\text{mA}} = 26\Omega$$

$$\therefore A_v = -\alpha \frac{R_C}{r_e} = -\frac{\beta}{1 + \beta} \cdot \frac{R_C}{r_e} = -\frac{150}{26} \cdot \frac{4\text{k}}{26} = -153$$

16. [Ans. D]


A positive noise spike can drive the voltage above 1.0 V level if the amplitude is greater than $V_{NL} = V_{IL(max)} - V_{OL(max)} = 1 - 0.1 = 0.9V$

A negative noise spike can drive the voltage below 3.5 V if the amplitude is greater than $V_{NH} = V_{OH(min)} - V_{IH(min)} = 4.9 - 3.5 = 1.4V$

17. [Ans. D]

May be 3,3+16,3+16+16 or 3+16+16+16+16

18. [Ans. D]

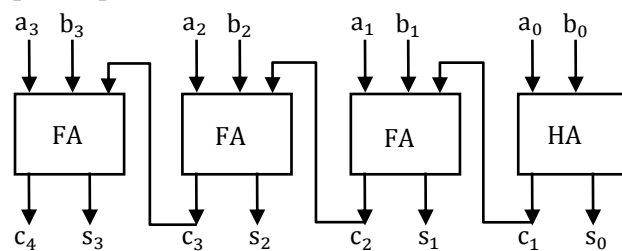

∴ No initial carry

≡ 3FA + 1HA

1FA = 2HA + 1-OR gate

3FA = 6HA + 3-OR gate

Total = 7HA + 3-OR gate

19. [Ans. C]

Method 1:

$R(s) = \frac{1}{s} \rightarrow$ Unit step

$C(s) = \frac{1}{s} + \frac{0.2}{s+60} - \frac{1.2}{s+10}$

$C(s) = \frac{s^2 + 70s + 600 + 0.2(s^2 + 10s) - 1.2(s^2 + 60s)}{s(s+60)(s+10)}$

$C(s) = \frac{600}{s[s^2 + 70s + 600]}$

Transfer Function = $\frac{C(s)}{R(s)} = \frac{600}{s^2 + 70s + 600}$

Standard equation \Rightarrow Transfer Function = $\frac{\omega_n^2}{s^2 + 70s + 600} = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$

$\omega_n = \sqrt{600} = 24.5 \text{ rad/s}$

$2\xi\omega_n = 70$

$\xi = \frac{70}{2 \times 24.5}$

$\xi = 1.42 \therefore \xi > 1 \rightarrow$ Over damped response

Method 2:

$\frac{C(s)}{R(s)} = \frac{600}{(s+10)(s+60)}$

System two real, negative and different poles so system is over damped

20. [Ans. *]Range: 0.99 to 1.01

Open Loop Transfer Function $G(s)H(s) = \frac{4}{s(s-2)}$

To construct Nyquist plot


$s_1 \Rightarrow$ Polar plot

$$G(j\omega)H(j\omega) = \frac{4}{j\omega(j\omega - 2)}$$

$$|G(j\omega)H(j\omega)| = \frac{4}{\omega\sqrt{\omega^2 + 4}}$$

$$\angle G(j\omega) = -90 - 180 + \tan^{-1}\left(\frac{\omega}{2}\right)$$

$\omega \rightarrow$	0		∞
$\angle G(j\omega)$	∞		0
$\angle G(j\omega)$	-270		-180

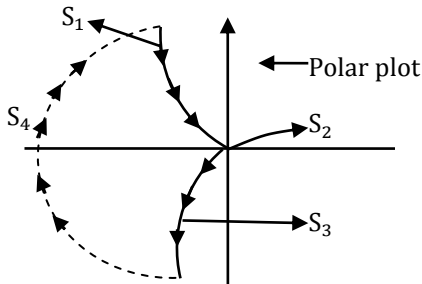

$s_2 \Rightarrow$ at origin

$s_3 \Rightarrow$ Inverse polar plot

$$s_4 \Rightarrow \text{Put } s = \lim_{R \rightarrow 0} R e^{j\theta} \rightarrow \left\{ \theta \Rightarrow \frac{-\pi}{2} \text{ to } \frac{+\pi}{2} \right\}$$

$$G(s) \Rightarrow \frac{4}{s(-2)}$$

$$-1 = e^{j\pi}$$

$$L(s) = \lim_{R \rightarrow 0} \frac{2}{R e^{j\theta} e^{j\pi}}$$

$$= \infty [e^{-j(\theta+\pi)}]$$

$$\Rightarrow \infty e^{-j\pi/2} \text{ to } e^{-j3\pi/2}$$

(One time encirclement in clockwise direction)

21. [Ans. C]

Let's say there is a source X having n symbols with entropy H(X)

$$0 \leq H(X) \leq \log_2 n$$

Entropy can be zero if any of the symbols has probability

22. [Ans.*]Range: 3.5 to 3.5

For PCM

$$R_b = n f_s$$

Where R_b = bit rate

n = number of bits required to encode a level

f_s = sampling frequency

$$\Rightarrow f_s = \frac{56 \times 10^6}{8} = 7 \times 10^6 \text{ Hz}$$

To avoid aliasing


$f_s \geq 2 f_m$, where f_m = message band with

$$\Rightarrow f_m \leq \frac{f_s}{2}$$

$$\Rightarrow f_m \leq 3.5 \times 10^6 \text{ Hz}$$


Hence maximum value of message bandwidth can be 3.5 MHz

23. [Ans. B]

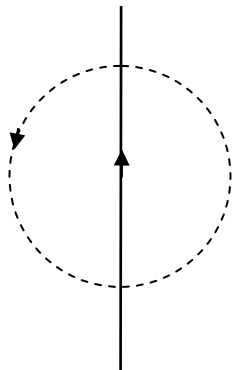

$$\oint_C \mathbf{H} \cdot d\mathbf{l} = I$$

Given,

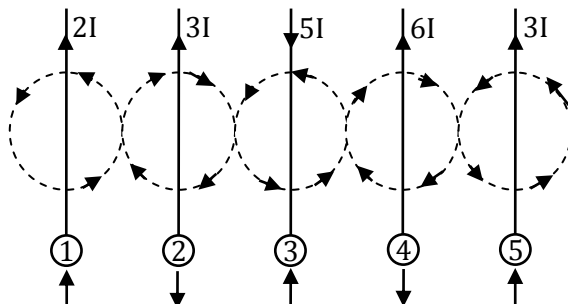

Actual Current,

$$I_{\text{Total}} \oint \mathbf{H} \cdot d\mathbf{l} = \oint \mathbf{H} \cdot d\mathbf{l} + \oint \mathbf{H} \cdot d\mathbf{l} + \oint \mathbf{H} \cdot d\mathbf{l} + \oint \mathbf{H} \cdot d\mathbf{l} + \oint \mathbf{H} \cdot d\mathbf{l}$$

Given Actual Direction is same: Positive current.

Given Actual Direction is same: Opposite negative current.

$$\therefore (2 - 3 - 5 - 6 + 3)I = -9I$$

24. [Ans. B]

From above equation

$$\omega = 10^8 \text{ rad/sec}$$

$$\beta = \frac{1}{\sqrt{3}} \text{ rad/m}$$

$$\therefore v = \frac{C}{\sqrt{\epsilon_r}} = \frac{\omega}{\beta}$$

$$\text{or } \frac{3 \times 10^8}{\sqrt{\epsilon_r}} = \frac{10^8}{\frac{1}{\sqrt{3}}}$$

$$\text{or, } \sqrt{3} = \sqrt{\epsilon_r}$$

$$\therefore \epsilon_r = 3$$

25. [Ans. C]

Number of modes of an optical fiber is obtained by cut off condition known as normalized frequency or V number. Therefore for this fiber,

$$\begin{aligned} \text{Number of modes} &= \frac{1}{2} |V|^2 \\ &= \frac{1}{2} \times 3.5^2 \\ &= 6.125 \end{aligned}$$

26. [Ans. D]

$$\text{Let } x = \sqrt{3}$$

$$x^2 = 3$$

$$x^2 - 3 = 0$$

$$f(x) = x^2 - 3$$

$$f'(x) = 2x$$

Newton Raphson's formula is

$$x_{n+1} = x_n - \frac{f(x_n)}{f'(x_n)}$$

$$x_{n+1} = x_n - \frac{x_n^2 - 3}{2x_n}$$

$$x_{n+1} = \frac{2x_n^2 - x_n^2 + 3}{2x_n}$$

$$x_{n+1} = \frac{x_n^2 + 3}{2x_n} = \frac{1}{2} \left[x_n + \frac{3}{x_n} \right]$$

27. [Ans. *] Range: 0 to 0

For odd 'n' order of matrix determinant of an $n \times n$ Skew symmetric matrix has the value 0.

28. [Ans. *] Range: 0.6 to 0.6

Problem is related to Binomial distribution with parameters $n = 3, p = 4/20$

Expected value for Binomial distribution is given by $np = 3(4/20) = 3/5 = 0.6$

(Or)

Let x denote number of defective items in the sample. The possible values of x and their mass function is given below.

X	0	1	2	3
$p(x = n)$	${}^3C_0 \left(\frac{4}{20}\right)^0 \left(\frac{16}{20}\right)^3$	${}^3C_1 \left(\frac{4}{20}\right)^1 \left(\frac{16}{20}\right)^2$	${}^3C_2 \left(\frac{4}{20}\right)^2 \left(\frac{16}{20}\right)^1$	${}^3C_3 \left(\frac{4}{20}\right)^3 \left(\frac{16}{20}\right)^0$

$$E(x) = 0.p(x = 0) + 1.p(x = 1) + 2.p(x = 2) + 3.p(x = 3)$$

$$= \frac{3}{5} = 0.6$$

29. [Ans. D]

1. We know that a linear system of equation is consistent when $\text{rank}(A/b) = \text{Rank}(A)$
option C is correct

2. $[0 \ 0 \ 0 \ \dots \ 0 | \alpha]$

$$\Rightarrow 0x_1 + 0x_2 + \dots + 0x_n = \alpha$$

There is no (x_1, x_2, \dots, x_n) satisfying


$$0x_1 + 0x_2 + \dots + 0x_n = \alpha$$

Option A is correct

3. 'B' does not contain a pivot. Hence b is a non-basic column in $[A/b]$

Hence Option D is correct

30. [Ans. *]Range: 32.4 to 32.6

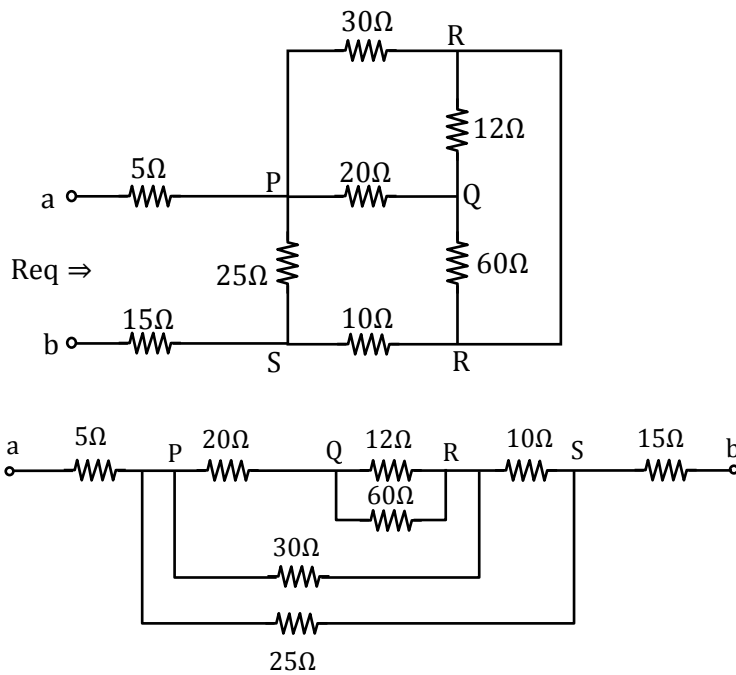

$$\text{Resistance}_{QR} = 12 \parallel 60 = 10\Omega$$

$$\text{Resistance}_{PR} = (10 + 20) \parallel 30 = 15\Omega$$

$$\text{Resistance}_{PS} = (15 + 10) \parallel 25 = 12.5\Omega$$

$$\text{Resistance}_{ab} = 5 + 12.5 + 15 = 32.5\Omega$$

31. [Ans. C]

Two port interconnection is series-shunt. So, we can add h-parameter to get net h-parameter.

$$z = \begin{bmatrix} 30 & 20 \\ 20 & 20 \end{bmatrix}$$

$$V_1 = 30i_1 + 20i_2 \dots\dots (i)$$

$$V_2 = 20i_1 + 20i_2 \dots\dots (ii)$$

h-parameter

$$V_1 = h_{11}i_1 + h_{12}V_2$$

$$i_2 = h_{21}i_1 + h_{22}V_2$$

$$h_{11} = \left. \frac{V_1}{i_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$

Put these conditions on the given parameter equation (i) and (ii)

$$V_2 = 0 \quad \text{Then } i_1 = -i_2$$

$$h_{21} = \frac{i_2}{i_1} = -1, \text{ from (i)}$$

$$V_1 = 30i_1 - 20i_1$$

$$V_1 = 10i_1$$

$$\frac{V_1}{i_1} = 10 = h_{11}$$

$$i_1 = 0$$

$$V_1 = 20i_2$$

$$V_2 = 20i_2$$

$$h_{12} = \frac{V_1}{V_2} = 1$$

$$h_{22} = \frac{i_2}{V_2} = \frac{1}{20}$$

$$h = \begin{bmatrix} 10 & 1 \\ -1 & \frac{1}{20} \end{bmatrix}$$

$$\text{Net } h = \begin{bmatrix} 20 & 2 \\ -2 & 0.1 \end{bmatrix}$$

32. [Ans. *]Range: 2.3 to 2.5

$$\frac{d^2y(t)}{dt^2} + \frac{3dy(t)}{dt} + 2y(t) = \frac{10dx(t)}{dt} + 15x(t)$$

Take L.T. both sides,

$$\frac{y(s)}{x(s)} = \frac{10s + 15}{s^2 + 3s + 2} = \frac{10s + 15}{(s + 1)(s + 2)}$$

$$H(s) = \frac{5}{s + 1} + \frac{5}{s + 2}$$

$$H(s) = (5e^{-t} + 5e^{-2t})u(t)$$

Sampling frequency=10 Hz

$$T_s = \frac{1}{10}$$

$$h(n) = (5e^{-nT_s} + 5e^{-2nT_s})u(n)$$

$$h(n) = (5e^{-0.1n} + 5e^{-0.2n})u(n)$$

$$H(z) = \left[\frac{5}{1 - e^{-0.1}z^{-1}} + \frac{5}{1 - e^{-0.2}z^{-1}} \right]$$

$$= \frac{10 - 5[e^{-0.2} + e^{-0.1}]z^{-1}}{1 - [e^{-0.1} + e^{-0.2}]z^{-1} + e^{-0.1}e^{-0.2}z^{-2}}$$

$$H(z) \Rightarrow \frac{10 - 5[e^{-0.2} + e^{-0.1}]z^{-1}}{1 - [1.722]z^{-1} + 0.740z^{-2}}$$

$$H(z) = \frac{10 - 8.61z^{-1}}{1 - az^{-1} + bz^{-2}}$$

$$a = 1.722$$

$$b = 0.740$$

$$a + b = 2.462$$

33. [Ans. *]Range: 0.99 to 1.01

$$x(n) = \{2, 1, 3, 1, 2, 0\}$$

↑

$$y(e^{j\omega}) = e^{j\omega}x(e^{j\omega})$$

$$\because x(n) \xleftrightarrow{\text{DTFT}} x(e^{j\omega})$$

$$\because x(n+1) \xleftrightarrow{\text{DTFT}} e^{j\omega}x(e^{j\omega})$$

$$\therefore y(n) = x(n+1)$$

$$y(n) = \{2, 1, 3, 1, 2, 0\}$$

↑

$$y(e^{j\omega}) = 2e^{+j\omega} + 1 + 3e^{-j\omega} + e^{-2j\omega} + 2e^{-3j\omega}$$

$$y(e^{j\omega}) = e^{-j\omega} [2e^{2j\omega} + e^{j\omega} + 3 + e^{-j\omega} + 2e^{-2j\omega}]$$

$$y(e^{j\omega}) = e^{-j\omega} [4 \cos 2\omega + 2 \cos \omega + 3]$$

$$y\left(e^{\frac{j\pi}{2}}\right) = e^{-\frac{j\pi}{2}} \left[4 \cos \frac{2\pi}{2} + 2 \cos \frac{\pi}{2} + 3\right]$$


$$y\left(e^{\frac{j\pi}{2}}\right) = -j[-4 + 0 + 3]$$

$$= -j[-1]$$

$$y\left(e^{\frac{j\pi}{2}}\right) = +j$$

$$y\left(e^{\frac{j\pi}{2}}\right) \Rightarrow 1$$

34. [Ans. C]

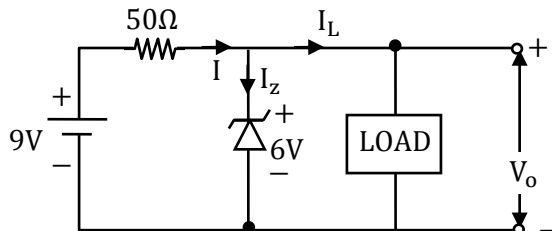

$$I = \frac{9 - 6}{50} = \frac{3}{50} = 60\text{mA}$$

Now when load current is maximum then

$$I_z = I_{\text{Knee}}$$

$$\therefore I_{\text{knee}} + I_{L\text{max}} = I$$

$$\Rightarrow 5 \text{ mA} + I_{L\text{max}} = 60\text{mA} \Rightarrow I_{L\text{max}} = 55\text{mA}$$

Now, maximum power dissipation in zener diode is

$$P_{z\text{max}} = V_z \cdot I_{z\text{max}}$$

$$\therefore I_{z\text{max}} = \frac{300\text{mW}}{6} = 50\text{mA}$$

When I_z is maximum then I_L will be minimum

$$\therefore I_{z\text{max}} + I_{L\text{min}} = 60 \text{ mA}$$

$$\therefore I_{L\text{min}} = 60\text{mA} - I_{z\text{max}} = 60 - 50 = 10 \text{ mA}$$

35. [Ans. *] Range: 70 to 72


$$n_{\text{surface}} = n_{\text{bulk}} e^{\frac{\psi_s}{\phi_t}}; \phi_t = \text{Thermal Voltage}$$

$$n_{\text{bulk}} = \frac{n_i^2}{NA} = \frac{(1.8 \times 10^{10})^2}{10^{17}}$$

$$n_{\text{surface}} = 3240 e^{0.2/26\text{m}}$$

$$= 7.1 \times 10^6 = 71 \times 10^5$$



36. [Ans. *] Range: 1.15 to 1.25

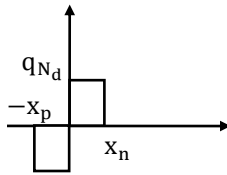

$$\frac{\partial E}{\partial x} = \frac{\rho_v}{\epsilon} = \frac{qN_d}{\epsilon}$$

$$E = \frac{-qN_d x_n}{\epsilon} \text{ [For n - side]}$$

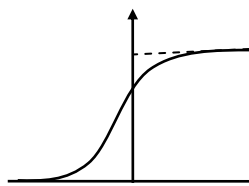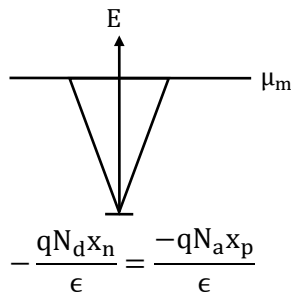
$$V = -\int E \cdot dl \text{ [Area Under curve of E]}$$



$$= -\frac{1}{2} \times \left(-\frac{qN_d x_n}{\epsilon} \right) (x_n + x_p)$$

$$= \frac{\frac{1}{2} \times 1.6 \times 10^{-19} \times 10^{17} \times 0.1 \times 10^{-4} \times 0.2 \times 10^{-4}}{15 \times 8.85 \times 10^{-14}} = 1.20 \text{ V}$$

37. [Ans. *]Range: 893 to 895

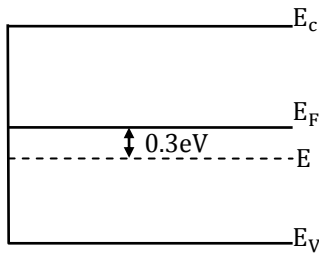

Probability to not have any electron below 0.32 eV than Fermi level is 0.02 . So probability to have an electron will be $1 - 0.02 = 0.98$

$$E_f - E = 0.3\text{ eV}$$

Now with Fermi probability distribution (Fermi Dirac function)

$$F(E) = \frac{1}{1 + e^{(E-E_f)/kT}} \text{ where } k \text{ is in eV/k}$$


$$0.98 = \frac{1}{1 + e^{\frac{-0.3}{kT}}} \quad k \left(\frac{\text{eV}}{\text{k}} \right) = \frac{1.38 \times 10^{-23}}{1.6 \times 10^{-19}} = 8.62 \times 10^{-5} \text{ eV/k}$$

$$0.98 e^{\frac{-0.3}{kT}} = 1 - 0.98$$

$$e^{\frac{-0.3}{kT}} = \frac{0.02}{0.98} \Rightarrow \frac{0.3}{kT} = 3.89$$

$$T = \frac{0.3}{3.89 \times 8.62 \times 10^{-5}} = 894.67 \approx 894$$

38. [Ans. C]

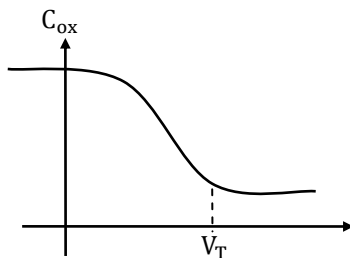

In first figure curve is becoming flatter at $V_{GB} = 2\text{ V}$

$$V_{T1} = 2\text{ V}$$

$$V_{T2} = 4\text{ V}$$

First one is having less threshold voltage which means less voltage required to generate inversion charge.

At any particular voltage first will generate more inversion charge compared to second one.

$$\text{So } V_{T1} < V_{T2} \text{ and } \theta_{i1} > \theta_{i2}$$

39. [Ans. A]

$$\frac{V_0}{V_i} = \frac{\frac{50 \times 10^3 \times \frac{1}{0.15 \times 10^{-6} j \omega}}{(50 \times 10^3) + \frac{1}{0.15 \times 10^{-6} j \omega}}}{50 \times 10^3 + \left(\frac{50 \times 10^3}{0.15 \times 10^{-6} \omega} \right) / \left[50 \times 10^3 + \frac{1}{0.15 \times 10^{-6} j \omega} \right]}$$

$$\Rightarrow \frac{V_0(j\omega)}{V_i(j\omega)} = \frac{10}{5 \times 0.15 \times 10^2 + 1 + 10}$$

putting $\omega = 100 \text{ rad/sec}$

$$\frac{V_0(j100)}{V_i(j100)} = \frac{10}{0.75j + 11}$$

$$\Rightarrow \left| \frac{V_0(j\omega)}{V_i(j\omega)} \right| = \frac{10}{\sqrt{(0.75)^2 + (11)^2}} = 11.02$$

$$V_m = \frac{10}{11.02} \times 1 \approx 1V$$

40. [Ans. A]

To determine the value of R_L that will turn the zener diode on

$$R_{L\min} = \frac{R V_z}{V_i - V_z} = \frac{1 \times 10}{50 - 10} = \frac{10k\Omega}{40} = 250\Omega$$

$$V_R = V_i - V_z = 40V$$

$$I_R = \frac{40}{1k\Omega} = 40 \text{ mA}$$

$$I_{L\min} = I_R - I_{zm} = 40 - 32 = 8 \text{ mA}$$

$$R_{L\max} = \frac{V_z}{I_{L\min}} = \frac{10V}{8 \text{ mA}} = 1.25k\Omega$$

41. [Ans.*]Range: 10 to 10

$$100 \text{ dB} = 10 \log_{10} \text{PSSR}$$

$$\Rightarrow \text{PSSR} = 10^{10}$$

$$\text{Power} \propto u^2$$

$$\text{So, } \text{VSSR} = \sqrt{10^{10}} = 10^5$$

$$\text{Now, } 10^5 = \frac{1 \text{ volt}}{\text{Input offset voltage}}$$

$$\Rightarrow \text{Input offset voltage} = \frac{1}{10^5} = 10\mu\text{V}$$

42. [Ans. B]

RST X

$$\text{Vector Address} = 8X = ()_{16}$$

$$\text{RST } 5.5 = 8 \times 5.5 = (44)_{10} = (002C)_H$$

43. [Ans. *]Range: 8 to 8

Maximum conversion time of an 8 bit digital ramp ADC is

$$2^n T_{CLK} = 2^8 \times 10 \mu \text{ sec} = 2560 \mu \text{ s} = T_1$$

Maximum conversion time of successive approximation ADC is

$$T_2 = n T_{CLK} = 8 \times 10 \mu \text{ s} = 80 \mu \text{ s}$$

Maximum conversion time of a flash types ADC is = T_{CLK}


$$T_3 = 10 \mu \text{ s}$$

$$P = \frac{T_1}{T_2} = 32$$

$$Q = \frac{T_1}{T_3} = 256$$

$$\frac{Q}{P} = \frac{256}{32} = 8$$

44. [Ans. B]

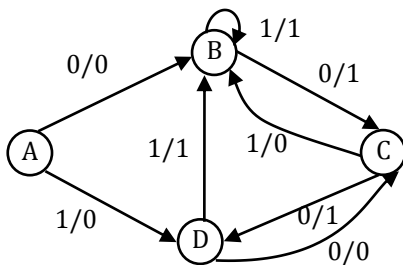

→ If A is start state, shortest sequence is 10 or 00 to reach C.


→ If B is start state, shortest sequence is 0 to reach C.

→ If C is start state, shortest sequence is 10 or 00 to reach C.

→ If D is start state, shortest sequence is 0 to reach C.

Option (B) is correct as no option are there only 0.

45. [Ans. *]Range: 1.67 to 1.71

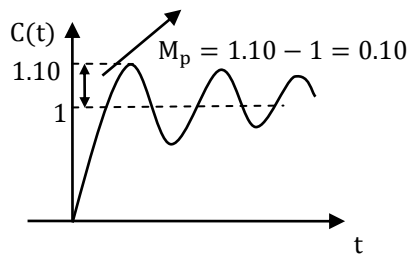

$$M_p = e^{-\xi\pi/\sqrt{1-\xi^2}} = 0.10$$

$$\xi = 0.59$$

$$\omega_d = 3.23 \text{ rad/s}$$

$$\omega_d = \omega_n \sqrt{1 - \xi^2}$$

$$3.23 = \omega_n \sqrt{1 - (0.59)^2}$$

$$\omega_n = 4 \text{ rad/s}$$

$$\text{settling time } t_s = \frac{4}{\xi\omega_n}$$

$$t_s = \frac{4}{0.59 \times 4}$$

$$t_s = 1.69$$

46. [Ans. A]

Magnitude

$$\left| \frac{2 - \omega^2}{\sqrt{\omega^2 + 1} \sqrt{\omega^2 + 9}} \right| = 0$$

$$2 - \omega^2 = 0$$

$$\omega = \pm\sqrt{2}$$

$$\omega = \sqrt{2} \text{ rad/sec}$$

47. [Ans. A]

From Diagram

Calculation of ω

$$5.105 \text{ dB} - 0 = -20[\log(\omega) - \log(90)]$$

$$5.105 = -20 \log(\omega) + 20 \log 90$$

$$5.105 = -20 \log(\omega) + 39.08$$

$$\omega \approx 50 \text{ r/s}$$

Calculation of k:

$$y - 5.105 = -40[\log(20) - \log(50)]$$

$$y - 5.105 = -52.04 + 67.95$$

$$y = 21.02 \text{ dB}$$

$$y = mx + c$$

$$21.02 = -20 \log(20) + c$$

$$21.02 = -26.02 + c$$


$$c = 47.021$$

$$c = 20 \log k$$

$$47.04 = 20 \log k$$

$$\Rightarrow k = 224.96$$


48. [Ans. B]

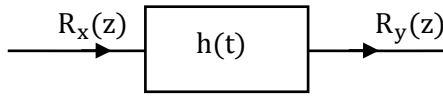

Where $R_x(z)$ and $R_y(z)$ are autocorrelation of $u(t)$ and $y(t)$ respectively $R_x(z) \xrightarrow{F.T} S_x(f)$

$$S_x(f) = \frac{N_0}{2}$$
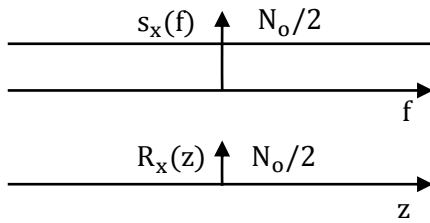
$$\Rightarrow R_x(z) = \frac{N_0}{2} \delta(z)$$



Now

$$R_y(z) = R_x(z) * h(z) * h(-z)$$

$$= \frac{N_0}{2} \delta(z) * h(z)h(-z)$$

$$= \frac{N_0}{2} \{h(z) * h(-z)\}$$

Since $R_H(z) = h(z) * h(-z)$ [Auto correlation of pulse $h(t)$]

$$\Rightarrow R_y(z) = \frac{N_0}{2} R_H(z)$$

$$\text{Now, o/p power} = R_y(0) = \frac{N_0}{2} R_H(0)$$

where $R_H(0)$ is the energy of the pulse $h(t)$

$$\Rightarrow R_H(0) = \int_0^2 h^2(t) dt = \frac{1}{4} \int_0^2 t^2 dt = \frac{1}{12} [t^3]_0^2 = \frac{2}{3}$$

$$\Rightarrow \text{o/p power} = \frac{2 N_0}{3 \cdot 2} = \frac{N_0}{3}$$

49. [Ans. C]

Without using raised cosine original band width = $\frac{2R_b}{M}$

Where R_b = bit rate

After using raise cosine

Band width = $\frac{\text{original Band width}}{2}(1 + \alpha)$

Where α = roll off factor

if excess band width = 50%

$\alpha = 0.5$

Now for distortion less transmission signal Band with \leq channel band with


$$\Rightarrow \frac{\frac{2R_b}{M}}{2}(1 + \alpha) \leq 3000$$

$$\Rightarrow \frac{16000}{3000} \times 6 \leq M$$

$$\Rightarrow M \geq 32$$


50. [Ans. *]Range: 1.5 to 1.5

$$x(t) = u(t) - u(t - 3)$$

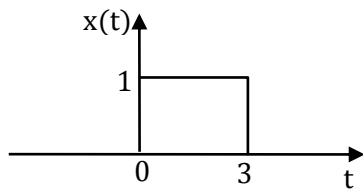

$$y(t) = x(-2t + 3)$$
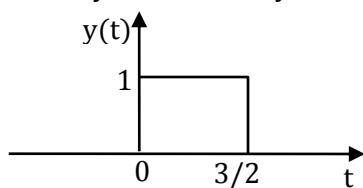
$$x(t) \xrightarrow[\text{by } 3]{\text{advance}} x(t + 3) \xrightarrow[\text{by } -2]{\text{Scale}} x(-2t + 3) = y(t)$$



$$R_y(0) = \text{Energy of } y(t) = \int_0^{3/2} y^2(t) dt$$

$$= \frac{3}{2} = 1.5$$

51. [Ans.*]Range: 1.5 to 1.6

We know

$$H(y) = P(y_1) \log_2 \left\{ \frac{1}{P(y_1)} \right\} + P(y_2) \log_2 \left\{ \frac{1}{P(y_2)} \right\} + P(y_3) \log_2 \left\{ \frac{1}{P(y_3)} \right\}$$

$$P(y_1) = P(x_1)P\left(\frac{y_1}{x_1}\right) + P(x_2)P\left(\frac{y_1}{x_2}\right)$$

$$\text{and } P\left(\frac{y_1}{x_1}\right) + P\left(\frac{y_2}{x_1}\right) + P\left(\frac{y_3}{x_1}\right) = 1$$

$$P\left(\frac{y_3}{x_1}\right) = \frac{1}{4}$$

$$\text{Similarly } P\left(\frac{y_1}{x_2}\right) = \frac{1}{2}$$

$$P(y_1) = \frac{1}{2} \times \frac{1}{4} + \frac{1}{2} \times \frac{1}{2} = \frac{3}{8}$$


$$\text{Similarly } P(y_2) = \frac{1}{2} \times \frac{1}{2} + \frac{1}{2} \times \frac{1}{4} = \frac{3}{8}$$

$$\text{and } P(y_3) = \frac{1}{2} \times \frac{1}{4} + \frac{1}{2} \times \frac{1}{4} = \frac{1}{4}$$

$$H(y) = - \left\{ \frac{3}{8} \log_2 \left(\frac{3}{8} \right) + \frac{3}{8} \log_2 \left(\frac{3}{8} \right) + \frac{1}{4} \log_2 \left(\frac{1}{4} \right) \right\}$$

$$= 1.561 \text{ bit/symbol}$$

52. [Ans.*] Range: 25.2 to 25.6

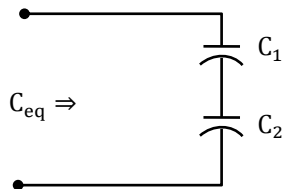

$$C_{eq} = \frac{C_1 + C_2}{C_1 C_2}$$

$$C_1 = \frac{\epsilon_1 A}{d_1}$$

$$C_2 = \frac{\epsilon_2 A}{d_2}$$

$$C_{eq} = \frac{\frac{\epsilon_1 A}{d_1} \frac{\epsilon_2 A}{d_2}}{\frac{\epsilon_1 A}{d_1} + \frac{\epsilon_2 A}{d_2}}$$

$$d_1 = d_2 = \frac{d}{2}$$

$$C_{eq} = \frac{2\epsilon_0 A}{d} \left[\frac{\epsilon_1 \epsilon_2}{\epsilon_1 + \epsilon_2} \right]$$

$$C_{eq} = \frac{2 \times 8.85 \times 10^{-12} \times 30 \times 10^{-4}}{5 \times 10^{-3}} \times \left[\frac{4 \times 6}{10} \right] = 25.488 \times 10^{-12}$$

$$C_{eq} = 25.48 \text{ pF}$$

53. [Ans. B]

$$Z_{oc} = 40\Omega$$

$$Z_{sc} = 5.625\Omega$$

$$Z_o = \sqrt{Z_{oc} \cdot Z_{sc}}$$

$$= \sqrt{40 \times 5.625}$$

$$= 15\Omega$$

$$Z_L = 50\Omega$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{12} = \frac{\pi}{6}$$

$$Z_{in} = Z_o \left[\frac{Z_L \cos \beta l + jZ_o \sin \beta l}{Z_o \cos \beta l + jZ_L \sin \beta l} \right]$$

$$= 15 \left[\frac{50 \times \frac{\sqrt{3}}{2} + j 15 \times \frac{1}{2}}{15 \times \frac{\sqrt{3}}{2} + j 50 \times \frac{1}{2}} \right]$$

$$\text{Find } \angle Z_{in} = \tan^{-1} \left(\frac{7.5}{25\sqrt{3}} \right) - \tan^{-1} \left(\frac{25}{7.5\sqrt{3}} \right)$$

$$= -0.92$$

Only (B) satisfies

54. [Ans. *]Range: 3.3 to 3.6

$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} e^{-2j\beta x}$$

$$|\Gamma| = \left| \frac{Z_L - Z_o}{Z_L + Z_o} \right|$$

$$= \left| \frac{j400}{600 + 400j} \right|$$

$$= \frac{400}{\sqrt{36 + 16}} = \frac{4}{\sqrt{52}} = 0.5547$$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 3.491$$

55. [Ans. A]

As the line charge lies along x direction $E_x = 0$

$$\text{Now, } \vec{E} = \frac{\rho_L}{2\pi\epsilon_0\rho} \vec{a}_\rho$$

$$\text{Where, } \vec{\rho} = (2 - 0)\vec{a}_y + (1 - 0)\vec{a}_z \\ = 2\vec{a}_y + \vec{a}_z$$

$$\therefore |\vec{\rho}| = \sqrt{2^2 + 1^2} = \sqrt{5}$$

$$\text{And, } \vec{a}_\rho = \frac{\vec{\rho}}{|\rho|} = \frac{2}{\sqrt{5}}\vec{a}_y + \frac{1}{\sqrt{5}}\vec{a}_z$$

$$\therefore \vec{E} = \frac{10 \times 10^{-6}}{2\pi \times 8.854 \times 10^{-12} \times \sqrt{5}} \cdot \left[\frac{2\vec{a}_y + \vec{a}_z}{\sqrt{5}} \right] \\ = 71.9\vec{a}_y + 35.97\vec{a}_z \text{ kV/m}$$