

GATE-2011

Question Paper

&


Answer Keys

Index

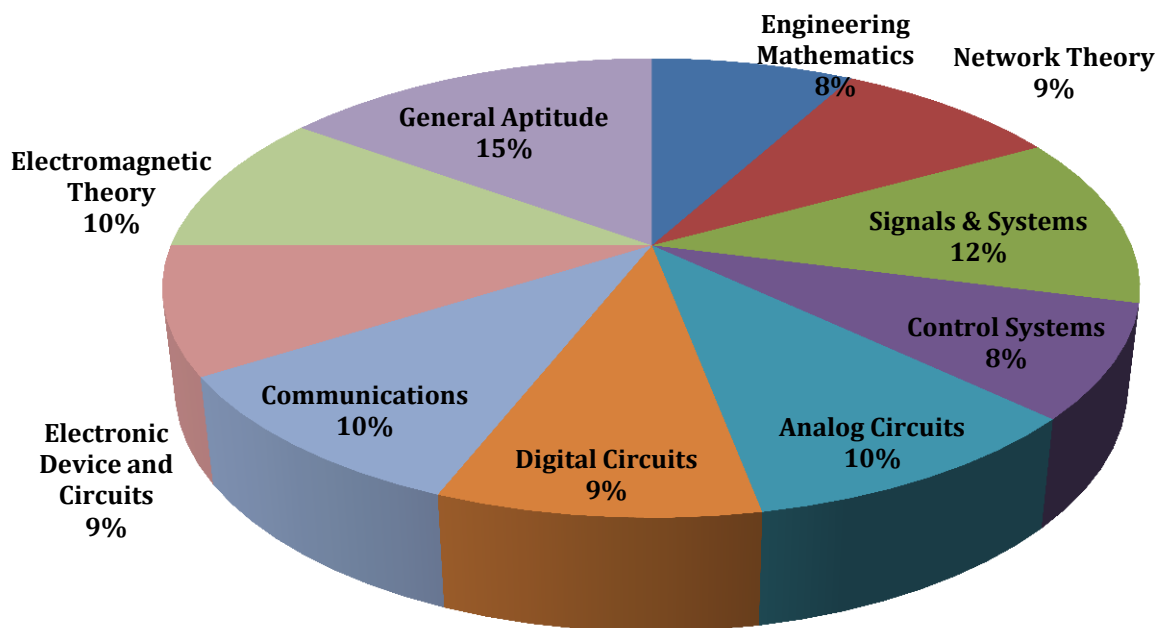1. Question Paper Analysis
2. Question Paper & Answer keys

ANALYSIS OF GATE 2011

Electronics and Communication Engineering



GATE-2011- ECE

| SUBJECT | NO OF QUESTION | Topics Asked in Paper | Total Marks |
|--------------------------------|-----------------------|--|--------------------|
| Engineering Mathematics | 1M:2 2M:3 | Linear Algebra, Probability & distribution Numerical Method, Differential Equations Complex Variables | 8 |
| Network Theory | 1M:3 2M:3 | Network Solution Methodology RLC Circuit-Transient/Steady State Analysis of RLC Circuits to dc Input Sinusoidal Steady State Analysis Two Port Net works | 9 |
| Signals & Systems | 1M:4 2M:4 | Introduction to Signals & Systems Fourier Representation of Signals Z-Transform, Laplace-Transform | 12 |
| Control Systems | 1M:2 2M:3 | Amplitude Modulation DS BSC , SSB & Vestigial sideband (VSB) modulation, Noise Analysis Digital communication | 8 |
| Analog Circuits | 1M:2 2M:4 | Diode Circuits-Analysis And Application DC Biasing-BJT's Small Signal Modeling Of BJT and FET Operational Amplifiers And Its Applications Feedback And Oscillator Circuits | 10 |
| Digital Circuits | 1M:3 2M:3 | Logic Gates Combinational and Sequential digital Circuits AD/DA Convertor, Introduction to Microprocessor | 9 |
| Communications | 1M:2 2M:4 | Amplitude Modulation DS BSC , SSB & Vestigial sideband (VSB) modulation Noise Analysis Digital communication | 10 |
| Electronic Device and Circuits | 1M:3 2M:3 | Semiconductor Theory P N Junction Theory & Characteristics Transistor Theory (BJT, FET) | 9 |
| Electromagnetic Theory | 1M:4 2M:3 | Electromagnetic fields, EM Wave propagation Transmission Lines, Guided E.M Waves | 10 |
| General Aptitude | 1M:5 2M:5 | Numerical Ability Verbal Ability | 15 |
| Total | 65 | | 100 |

GATE 2011 Examination

Electronics and Communication Engineering

Q.1 - Q.25 Carry One Mark each.

1. The modes in a rectangular waveguide are denoted by TE_{mn}/TM_{mn} where m and n are the Eigen numbers along the larger and smaller dimensions of the waveguide respectively. Which one of the following statements is **TRUE**?
- (A) The TM_{10} mode of the waveguide does not exist
 - (B) The TE_{10} mode of the waveguide does not exist
 - (C) The TM_{10} and the TE_{10} modes both exist and have the same cut – off frequencies
 - (D) The TM_{10} and the TM_{01} modes both exist and have the same cut – off frequencies
- [Ans. A]**

2. The list-I the attributes and the list-II the modulation system. Match the attribute to the modulation system that best meets it.

List-I

- P. Power efficient transmission signals
- Q. Most bandwidth efficient transmission of voice signals
- R. Simplest receiver structure
- S. Bandwidth efficient transmission of Signals with significant dc component

List-II



- i. Conventional AM
- ii. FM
- iii. VSB
- iv. SSB-SC



Codes:

- (A) P-iv, Q-ii, R-i, S-iii
- (B) P-ii, Q-iv, R-i, S-iii
- (C) P-iii, Q-ii, R-i, S-iv
- (D) P-ii, Q-iv, R-iii, S-i

[Ans. B]

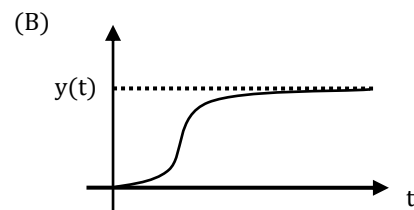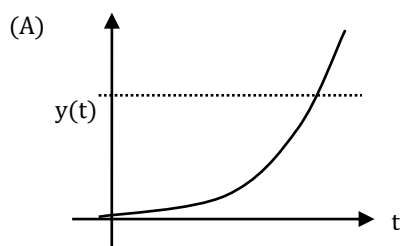3. The differential equation $100 \frac{d^2y}{dt^2} - 20 \frac{dy}{dt} + y = x(t)$ describes a system with an input $x(t)$ and an output $y(t)$. The system, which is initially relaxed, is excited by a unit step input. The output $y(t)$ can be represented by the waveform







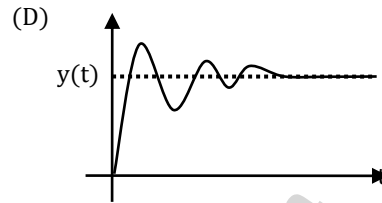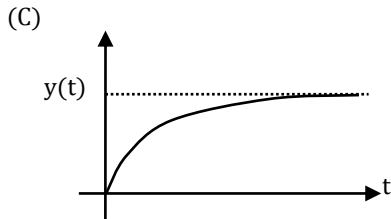

[Ans. A]

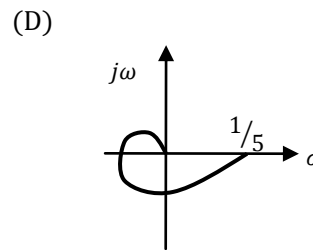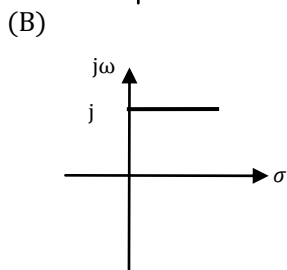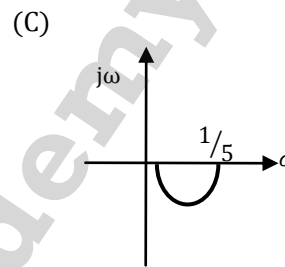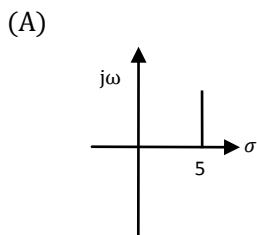4. For the transfer function

$G(j\omega) = 5 + j\omega$, the corresponding Nyquist plot for the positive frequency has the form



[Ans. A]

5. The trigonometric Fourier series of an even function does not have the

(A) Dc term


(C) Sine terms

(B) Cosine terms

(D) Odd harmonic terms

[Ans. C]

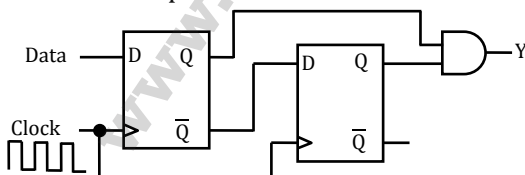6. When the output Y in the circuit below is "1", it implies that data has



(A) Changed from "0" to "1"


(C) Changed in either direction

(B) Changed from "1" to "0"

(D) Not changed

[Ans. A]

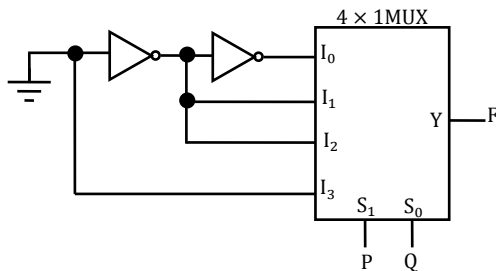
7. The logic function implemented by the circuit below is (ground implies a logic “0”)



- (A) $F = \text{AND}(P, Q)$ (C) $F = \text{XNOR}(P, Q)$
 (B) $F = \text{OR}(P, Q)$ (D) $F = \text{XOR}(P, Q)$

[Ans. D]

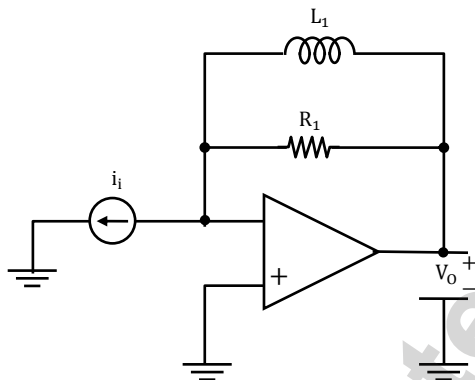8. The circuit below implements a filter between the input current i_i and the output voltage v_o . Assume that the opamp is ideal. The filter implemented is a



- (A) low pass filter (C) band stop filter
 (B) band pass filter (D) high pass filter


[Ans. D]

9. A silicon PN junction is forward biased with a constant current at room temperature. When the temperature is increased by 10°C , the forward bias voltage across the PN junction

- (A) Increases by 60 mv (C) Increases by 25 mv
 (B) Decreases by 60 mv (D) Decreases by 25 mv

[Ans. D]

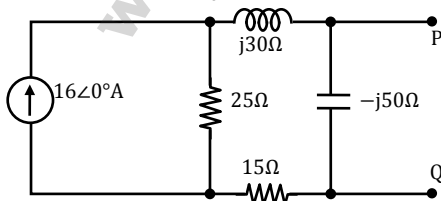
10. In the circuit shown below, the Norton equivalent current in amperes with respect to the terminals P and Q is



- (A) $6.4 - j4.8$ (C) $10 + j0$
 (B) $6.56 - j7.87$ (D) $16 + j0$

[Ans. A]

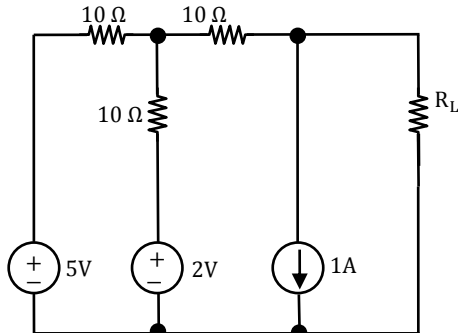11. In the circuit shown below, the value of R_L such that the power transferred to R_L is maximum is



- (A) 5Ω (C) 15Ω
(B) 10Ω (D) 20Ω
[Ans. C]


12. The value of the integral $\oint_C \frac{-3z+4}{(z^2+4z+5)} dz$ where c is the circle $|z| = 1$ is given by
(A) 0 (C) $4/5$
(B) $1/10$ (D) 1
[Ans. A]

13. A transmission line of characteristic impedance 50Ω is terminated by a 50Ω load. When excited by a sinusoidal voltage source at 10 GHz, the phase difference between two points spaced 2 mm apart on the line is found to be $\pi/4$ radians. The phase velocity of the wave along the line is
(A) 0.8×10^8 m/s (C) 1.6×10^8 m/s
(B) 1.2×10^8 m/s (D) 3×10^8 m/s
[Ans. C]

14. Consider the following statements regarding the complex Poynting vector \vec{P} for the power radiated by a point source in an infinite homogeneous and lossless medium $\text{Re}(\vec{P})$ denotes the real part of \vec{P} , S denotes a spherical surface whose centre is at the point source, and \hat{n} denotes the unit surface normal on S . Which of the following statements is **TRUE**?
(A) $\text{Re}(\vec{P})$ remains constant at any radial distance for the source
(B) $\text{Re}(\vec{P})$ increases with increasing radial distance from the source
(C) $\oint_S \text{Re}(\vec{P}) \cdot \hat{n} dS$ remains constant at any radial distance from the source
(D) $\oint_S \text{Re}(\vec{P}) \cdot \hat{n} dS$ decreases with increasing radial distance from the source
[Ans. C]

15. An analog signal is band-limited to 4 KHz. Sampled at the Nyquist rate and the samples are quantized into 4 levels. The quantized levels are assumed to be independent and equally probable. If we transmit two quantized samples per second, the information rate is
(A) 1 bit/sec (C) 3 bits/sec
(B) 2 bits/sec (D) 4 bits/sec
[Ans. D]

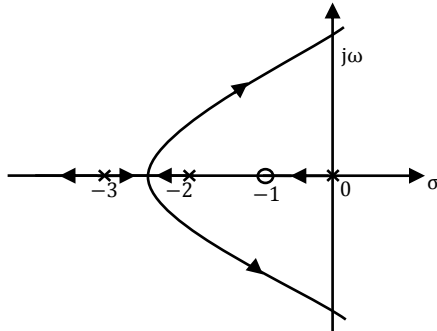16. The root locus plot for a system is given below. The open loop transfer function corresponding to this plot is given by



- (A) $G(s)H(s) = k \frac{s(s+1)}{(s+2)(s+3)}$ (C) $G(s)H(s) = k \frac{1}{s(s-1)(s+2)(s+3)}$
 (B) $G(s)H(s) = k \frac{(s+1)}{s(s+2)(s+3)^2}$ (D) $G(s)H(s) = k \frac{(s+1)}{s(s+2)s+3}$

[Ans. B]


17. A system is defined by its impulse response $h(n) = 2^n u(n-2)$. The system is
 (A) Stable and causal (C) Stable but not causal
 (B) Causal but not stable (D) Unstable and non-causal

[Ans. B]

18. If the unit step response of a network is $(1 - e^{-\alpha t})$, then its unit impulse response is
 (A) $\alpha e^{-\alpha t}$ (C) $(1 - \alpha^{-1})e^{-\alpha t}$
 (B) $\alpha^{-1}e^{-\alpha t}$ (D) $(1 - \alpha)e^{-\alpha t}$

[Ans. A]

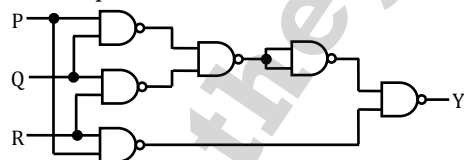
19. The output Y in the circuit below is always “1” when



- (A) Two or more of the inputs P, Q, R are “0”
 (B) Two or more of the inputs P, Q, R are “1”
 (C) Any odd number of the inputs P, Q, R is “0”
 (D) Any odd number of the inputs P, Q, R is “1”

[Ans. B]

20. In the circuit shown below, capacitors C_1 and C_2 are very large and are shorts at the input frequency. v_i is a small signal input. The gain magnitude $|v_o/v_i|$ at 10 Mrad/s is

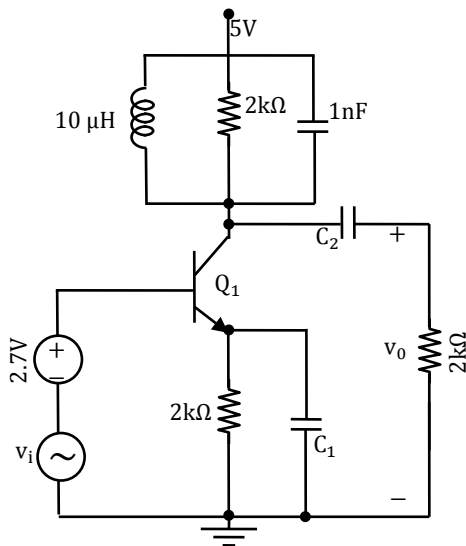


- (A) Maximum
(B) Minimum
(C) Unity
(D) Zero
- [Ans. A]

21. Drift current in semiconductors depends upon
- (A) Only the electric field
(B) Only the carrier concentration gradient
(C) Both the electric field and the carrier concentration
(D) Both the electric field and the carrier concentration gradient
- [Ans. C]

22. A Zener diode, when used in voltage stabilization circuits, is biased in
- (A) reverse bias region below the breakdown voltage
(B) reverse breakdown region
(C) forward bias region
(D) forward bias constant current mode
- [Ans. B]

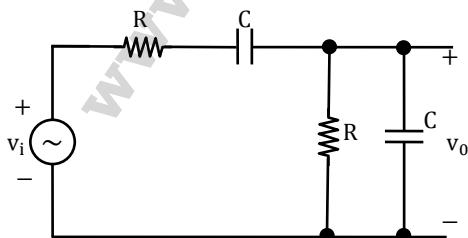23. The circuit shown below is driven by a sinusoidal input $v_i = V_p \cos(t/RC)$. The steady state output v_o is



- (A) $(V_p/3) \cos(t/RC)$
(B) $(V_p/3) \sin(t/RC)$
(C) $(V_p/2) \cos(t/RC)$
(D) $(V_p/2) \sin(t/RC)$
- [Ans. A]

24. Consider a closed surface S surrounding a volume V . If \vec{r} is the position vector of a point inside S , with \hat{n} the unit normal on S , the value of the integral $\oint_S 5\vec{r} \cdot \hat{n} \, dS$ is
 (A) 3V (B) 5V (C) 10V (D) 15V

[Ans. D]

25. The solution of the differential equation $\frac{dy}{dx} = ky$, $y(0) = c$ is
 (A) $x = ce^{-ky}$ (C) $y = ce^{kx}$
 (B) $x = ke^{cy}$ (D) $y = ce^{-kx}$

[Ans. C]

Q.26 - Q.55 Carry Two Mark each.

26. The electric and magnetic fields for a TEM wave of frequency 14 GHz in a homogeneous medium of relative permittivity ϵ_r and relative permeability $\mu_r = 1$ are given by

$$\vec{E} = E_p e^{j(\omega t - 280\pi y)} \hat{u}_z \text{ V/m}$$

$$\vec{H} = 3e^{j(\omega t - 280\pi y)} \hat{u}_x \text{ A/m}$$

Assuming the speed of light in free space to be 3×10^8 m/s, the intrinsic impedance of free space to be 120π , the relative permittivity ϵ_r of the medium and the electric field amplitude E_p are

- (A) $\epsilon_r = 3, E_p = 120\pi$ (C) $\epsilon_r = 9, E_p = 360\pi$
 (B) $\epsilon_r = 3, E_p = 360\pi$ (D) $\epsilon_r = 9, E_p = 120\pi$


[Ans. D]

27. A message signal $m(t) = \cos 2000\pi t + 4 \cos 4000\pi t$ modulates the carrier $c(t) = \cos 2\pi f_c t$ where $f_c = 1\text{MHz}$ to produce an AM signal. For demodulating the generated AM signal using an envelope detector, the time constant RC of the detector circuit should satisfy.

- (A) $0.5 \text{ ms} < RC < 1 \text{ ms}$ (C) $RC \ll 1 \mu\text{s}$
 (B) $1 \mu\text{s} \ll RC \ll 0.5 \text{ ms}$ (D) $RC \gg 0.5 \text{ ms}$

[Ans. B]

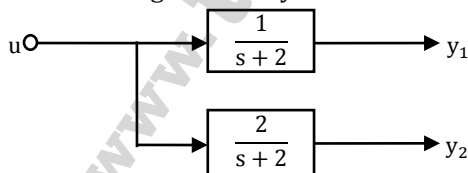28. The block diagram of a system with one input u and two outputs y_1 and y_2 is given below.




A state space model of the above system in terms of the state vector \underline{x} and the output vector $\underline{y} = [y_1 \ y_2]^T$ is

- (A) $\dot{\underline{x}} = [2]\underline{x} + [1]u; \underline{y} = [1 \ 2]\underline{x}$
 (B) $\dot{\underline{x}} = [-2]\underline{x} + [1]u; \underline{y} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} \underline{x}$
 (C) $\dot{\underline{x}} = \begin{bmatrix} -2 & 0 \\ 0 & -2 \end{bmatrix} \underline{x} + \begin{bmatrix} 1 \\ 1 \end{bmatrix} u; \underline{y} = [1 \ 2]\underline{x}$
 (D) $\dot{\underline{x}} = \begin{bmatrix} 2 & 0 \\ 0 & 2 \end{bmatrix} \underline{x} + \begin{bmatrix} 1 \\ 1 \end{bmatrix} u; \underline{y} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} \underline{x}$

[Ans. B]

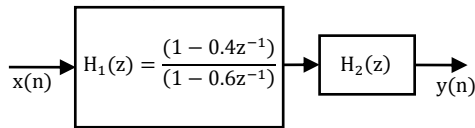29. Two systems $H_1(z)$ and $H_2(z)$ are connected in cascade as shown below. The overall output $y(n)$ is the same as the input $x(n)$ with a one unit delay. The transfer function of the second system $H_2(z)$ is



- (A) $\frac{(1 - 0.6z^{-1})}{z^{-1}(1 - 0.4z^{-1})}$ (C) $\frac{z^{-1}(1 - 0.4z^{-1})}{(1 - 0.6z^{-1})}$
 (B) $\frac{z^{-1}(1 - 0.6z^{-1})}{(1 - 0.4z^{-1})}$ (D) $\frac{(1 - 0.4z^{-1})}{z^{-1}(1 - 0.6z^{-1})}$

[Ans. B]

30. An 8085 assembly language program is given below. Assume that the carry flag is initially unset. The content of the accumulator after the execution of the program is

```
MVI  A, 07H
RLC
MOV  B, A
RLC
RLC
ADD  B
RRC
```

- (A) 8CH (B) 64H (C) 23H (D) 15H


[Ans. C]

31. The first six points of the 8-point DFT of a real valued sequence are 5, $1-j3$, 0, $3-j4$, 0 and $3+j4$. The last two points of the DFT are respectively

- (A) 0, $1-j3$ (B) 0, $1+j3$ (C) $1-j3$, 5 (D) $1+j3$, 5

[Ans. B]

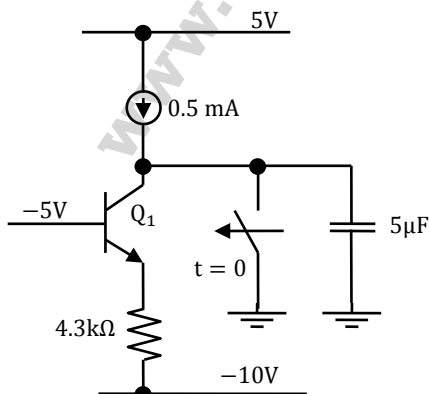32. For the BJT Q_1 in the circuit shown below, $\beta = \infty$, $V_{BE_{on}} = 0.7V$, $V_{CE_{sat}} = 0.7V$. The switch is initially closed. At time $t = 0$, the switch is opened. The time t at which Q_1 leaves the active region is




- (A) 10 ms (B) 25 ms (C) 50 ms (D) 100 ms

[Ans. B]

33. In the circuit shown below, the network N is described by the following Y matrix:

$$Y = \begin{bmatrix} 0.1 \text{ S} & -0.01 \text{ S} \\ 0.01 \text{ S} & 0.1 \text{ S} \end{bmatrix}$$


The voltage gain $\frac{V_2}{V_1}$ is

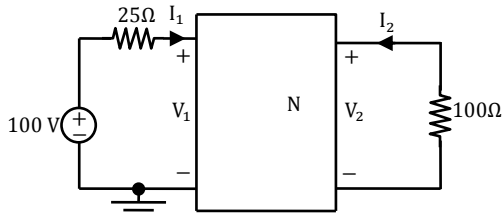

- (A) $1/90$ (C) $-1/99$
(B) $-1/90$ (D) $-1/11$

[Ans. D]

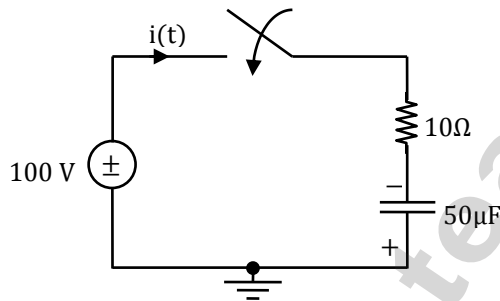34. In the circuit shown below, the initial charge on the capacitor is 2.5 mC, with the voltage polarity as indicated. The switch is closed at time $t = 0$. The current $i(t)$ at a time t after the switch is closed is



- (A) $i(t) = 15 \exp(-2 \times 10^3 t) \text{ A}$ (C) $i(t) = 10 \exp(-2 \times 10^3 t) \text{ A}$
(B) $i(t) = 5 \exp(-2 \times 10^3 t) \text{ A}$ (D) $i(t) = -5 \exp(-2 \times 10^3 t) \text{ A}$

[Ans. A]

35. The system of equations
 $x + y + z = 6$
 $x + 4y + 6z = 20$
 $x + 4y + \lambda z = \mu$
 has NO solution for values of λ and μ given by

- (A) $\lambda = 6, \mu = 20$ (C) $\lambda \neq 6, \mu = 20$
(B) $\lambda = 6, \mu \neq 20$ (D) $\lambda \neq 6, \mu \neq 20$

[Ans. B]


36. A fair dice is tossed two times. The probability that the second toss results in a value that is higher than the first toss is

- (A) $2/36$ (C) $5/12$
(B) $2/6$ (D) $1/2$

[Ans. C]

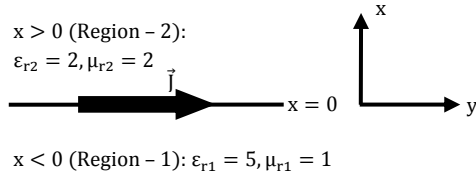37. A current sheet $\vec{J} = 10\hat{u}_y \text{ A/m}$ lies on the dielectric interface $x = 0$ between two dielectric media with $\epsilon_{r1} = 5, \mu_{r1} = 1$ in Region - 1 ($x < 0$) and $\epsilon_{r2} = 2, \mu_{r2} = 2$ in Region - 2 ($x > 0$). If the magnetic field in Region - 1 at $x = 0^-$ is

$\vec{H}_1 = 3\hat{u}_x + 30\hat{u}_y$ A/m, the magnetic field in Region - 2 at $x = 0^+$ is



- (A) $\vec{H}_2 = 1.5\hat{u}_x + 30\hat{u}_y - 10\hat{u}_z$ A/m
 (B) $\vec{H}_2 = 3\hat{u}_x + 30\hat{u}_y - 10\hat{u}_z$ A/m
 (C) $\vec{H}_2 = 1.5\hat{u}_x + 40\hat{u}_y$ A/m
 (D) $\vec{H}_2 = 3\hat{u}_x + 30\hat{u}_y + 10\hat{u}_z$ A/m


[Ans. A]

38. A transmission line of characteristic impedance 50Ω is terminated in a load impedance Z_L . The VSWR of the line is measured as 5 and the first of the voltage maxima in the line is observed at a distance of $\lambda/4$ from the load. The value of Z_L is

- (A) 10Ω
 (B) 250Ω
 (C) $(19.23 + j46.15) \Omega$
 (D) $(19.23 - j46.15) \Omega$

[Ans. A]



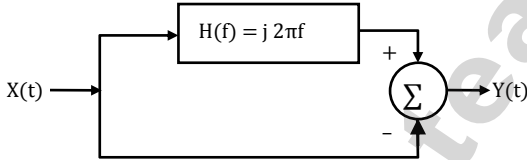
39. $X(t)$ is a stationary random process with autocorrelation function $R_x(\tau) = \exp(-\pi\tau^2)$. This process passed through the system shown below. The power spectral density of the output process $Y(t)$ is





- (A) $(4\pi^2 f^2 + 1) \exp(-\pi f^2)$
 (B) $(4\pi^2 f^2 - 1) \exp(-\pi f^2)$
 (C) $(4\pi^2 f^2 + 1) \exp(-\pi f)$
 (D) $(4\pi^2 f^2 - 1) \exp(-\pi f)$

[Ans. A]

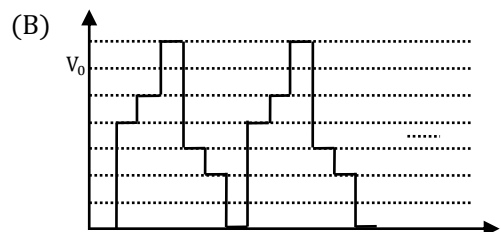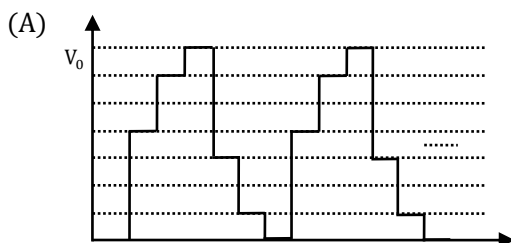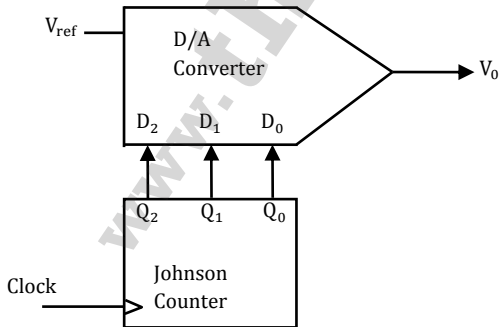40. The output of a 3 - stage Johnson (twisted - ring) counter is fed to a digital - to - analog (D/A) converter as shown in the figure below. Assume all states of the counter to be unset initially. The waveform which represents the D/A converter output V_0 is



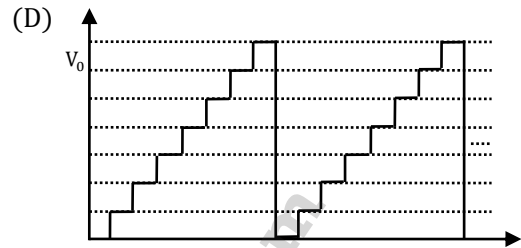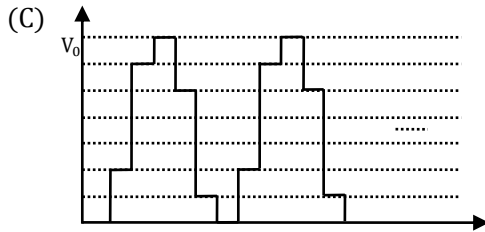

[Ans. A]


41. Two D flip - flops are connected as a synchronous counter that goes through the following $Q_B Q_A$ sequence $00 \rightarrow 11 \rightarrow 01 \rightarrow 10 \rightarrow 00 \rightarrow \dots$
The connections to the inputs D_A and D_B are

- (A) $D_A = Q_B, D_B = Q_A$
(B) $D_A = \bar{Q}_A, D_B = \bar{Q}_B$

- (C) $D_A = (Q_A \bar{Q}_B + \bar{Q}_A Q_B), D_B = Q_A$
(D) $D_A = (Q_A Q_B + \bar{Q}_A \bar{Q}_B), D_B = \bar{Q}_B$

[Ans. D]

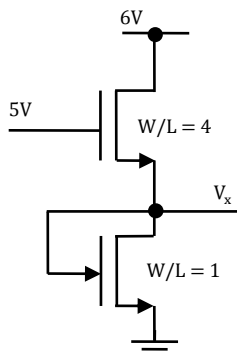42. In the circuit shown below, for the MOS transistor, $\mu_n C_{ox} = 100 \mu A/V^2$ and the threshold voltage $V_T = 1V$. The voltage V_x at the source of the upper transistor is



- (A) 1 V (C) 3 V
(B) 2 V (D) 3.67 V

[Ans. C]

43. An input $x(t) = \exp(-2t)u(t) + \delta(t - 6)$ is applied to an LTI system with impulse response $h(t) = u(t)$. The output is

- (A) $[1 - \exp(-2t)]u(t) + u(t + 6)$
(B) $[1 - \exp(-2t)]u(t) + u(t - 6)$
(C) $0.5[1 - \exp(-2t)]u(t) + u(t + 6)$
(D) $0.5[1 - \exp(-2t)]u(t) + u(t - 6)$

[Ans. D]

44. For a BJT, the common - base current gain $\alpha = 0.98$ and the collector base junction reverse bias saturation current $I_{C0} = 0.6 \mu A$. This BJT is connected in the common emitter mode and operated in the active region with a base drive current $I_B = 20 \mu A$. The collector current I_C for this mode of operation is

- (A) 0.98 mA (C) 1.0 mA
(B) 0.99 mA (D) 1.01 mA


[Ans. D]

45. If $F(s) = \mathcal{L}[f(t)] = \frac{2(s+1)}{s^2+4s+7}$ then the initial and final values of $f(t)$ are respectively

- (A) 0, 2 (C) 0, 2/7
(B) 2, 0 (D) 2/7, 0

[Ans. B]

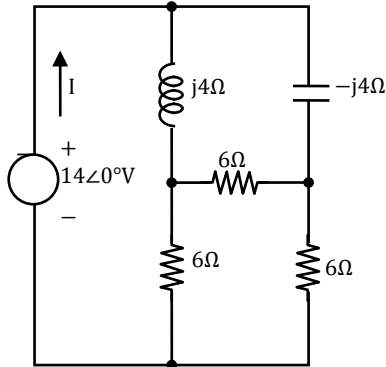46. In the circuit shown below, the current I is equal to



- (A) $1.4 \angle 0^\circ$ A (C) $2.8 \angle 0^\circ$ A
(B) $2.0 \angle 0^\circ$ A (D) $3.2 \angle 0^\circ$ A

[Ans. B]


47. A numerical solution of the equation $f(x) = x + \sqrt{x} - 3 = 0$ can be obtained using Newton - Raphson method. If the starting value is $x = 2$ for the iteration, the value of x that is to be used in the next step is

- (A) 0.306 (C) 1.694
(B) 0.739 (D) 2.306

[Ans. C]

Common Data for Q. No 48 and 49

The channel resistance of an N-channel JFET shown in the figure below is 600Ω when the full channel thickness (t_{ch}) of $10 \mu\text{m}$ is available for conduction. The built-in voltage of the gate P+N junction (V_{bi}) is -1V . When the gate to source voltage (V_{GS}) is 0V , the channel is depleted by $1 \mu\text{m}$ on each side due to the built-in voltage and hence the thickness available for conduction is only $8 \mu\text{m}$

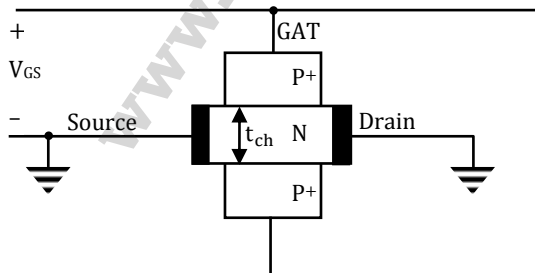

48. The channel resistance when $V_{GS} = 0\text{V}$ is

- (A) 480Ω (C) 750Ω
(B) 600Ω (D) 1000Ω


[Ans. C]

49. The channel resistance when $V_{GS} = -3 \text{ V}$ is
 (A) 360Ω (C) 1000Ω
 (B) 917Ω (D) 3000Ω


[Ans. C]

Common Data for Q.No 50 and 51

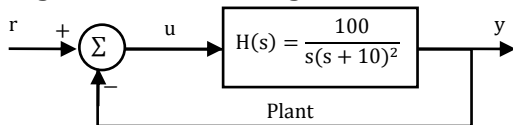The input - output transfer function of a plant $H(s) = \frac{100}{s(s+10)^2}$. The plant is placed in a unity negative feedback configuration as shown in the figure below.



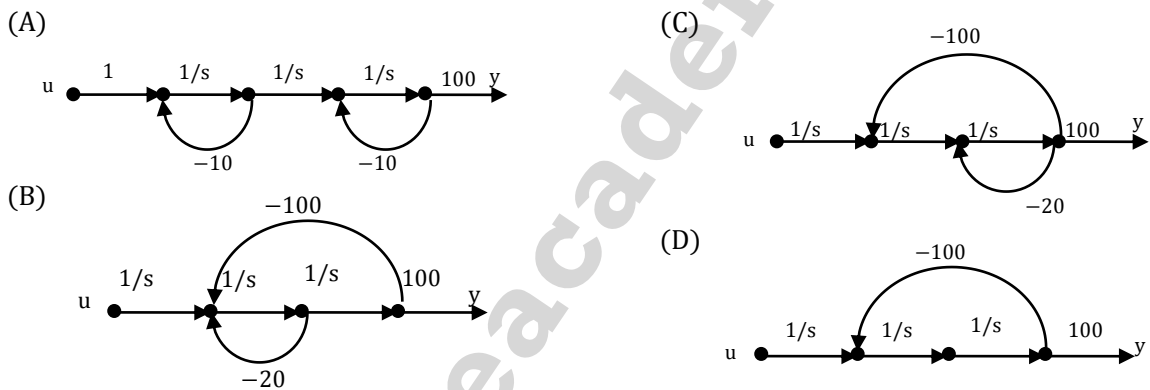50. The signal flow graph that DOES NOT model the plant transfer function $H(s)$ is




[Ans. D]

51. The gain margin of the system under closed loop unity negative feedback is
 (A) 0 dB (C) 26 dB
 (B) 20 dB (D) 46 dB

[Ans. C]

Statement for Linked Question 52 and 53

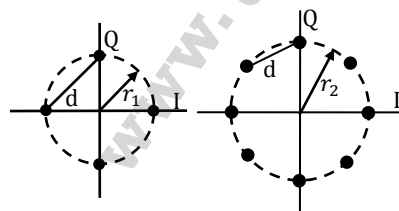A four-phase and an eight-phase signal constellation are shown in the figure below.




52. For the constraint that the minimum distance between pairs of signal points be d for both constellations, the radii r_1 and r_2 of the circles are
 (A) $r_1 = 0.707d, r_2 = 2.782d$ (C) $r_1 = 0.707d, r_2 = 1.545d$
 (B) $r_1 = 0.707d, r_2 = 1.932d$ (D) $r_1 = 0.707d, r_2 = 1.307d$

[Ans. D]

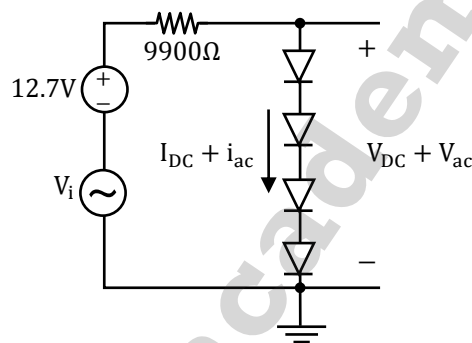53. Assuming high SNR and that all signals are equally probable, the additional average transmitted signal energy required by the 8-PSK signal to achieve the same error probability as the 4-PSK signal is
- (A) 11.90 dB (C) 6.79 dB
(B) 8.73 dB (D) 5.33 dB
- [Ans. D]**

Statements for Linked Answer Q. No 54 & 55

In the circuit shown below, assume that the voltage drop across a forward biased diode is 0.7V. The thermal voltage $V_t = \frac{kT}{q} = 25\text{mV}$. The small signal input $v_i = V_p \cos(\omega t)$ where $V_p = 100\text{mV}$.



54. The bias current I_{DC} through the diodes is
- (A) 1 mA (C) 1.5 mA
(B) 1.28 mA (D) 2 mA
- [Ans. A]**
55. The ac output voltage v_{ac} is
- (A) $0.25 \cos(\omega t)$ mV (C) $2 \cos(\omega t)$ mV
(B) $1 \cos(\omega t)$ mV (D) $22 \cos(\omega t)$ mV
- [Ans. B]**

General Aptitude One Marks Question Q. 56 to Q. 60

56. The question below consists of a pair of related words followed by four pairs of words. Select the pair that best expresses the relation in the original pair:
Gladiator: Arena
- (A) dancer: stage (C) teacher: classroom
(B) commuter: train (D) lawyer: courtroom
- [Ans. D]**
57. There are two candidates P and Q in an election. During the campaign, 40% of the voters promised to vote for P, and rest for Q. However, on the day of election 15% of the voters went back on their promise to vote for P and instead voted for Q. 25% of the voters went back on their promise to vote for Q and instead voted for P. Suppose, P lost by 2 votes, then what was the total number of voters?
- (A) 100 (C) 90
(B) 110 (D) 95
- [Ans. A]**

58. Choose the most appropriate word from the options given below to complete the following sentence:

It was her view that the country's problems had been by foreign technocrats, so that to invite them to come back would be counter-productive.

- (A) Identified (C) Texacerbated
(B) Ascertained (D) Analysed

[Ans. C]

59. Choose the word from the options given below that is most nearly opposite in meaning to the given word:

Frequency

- (A) periodicity (C) gradualness
(B) rarity (D) persistency

[Ans. B]

60. Choose the most appropriate word from the options given below to complete the following sentence: Under ethical guidelines recently adopted by the Indian Medical Association, human genes are to be manipulated only to correct _____ diseases for which unsatisfactory.

- (A) Similar (C) Uncommo
(B) Most (D) Available

[Ans. D]


General Aptitude Two Marks Question Q. 61 to Q. 65

61. The horse has played a little known but very important role in the field of medicine. Horses were injected with toxins of diseases until their blood built up immunities. Then a serum was made from their blood. Serums to fight with diphtheria and tetanus were developed this way. It can be inferred from the passage that horses were

- (A) given immunity to diseases
(B) generally quite immune to diseases
(C) given medicines to fight toxins
(D) given diphtheria and tetanus serums

[Ans. B]

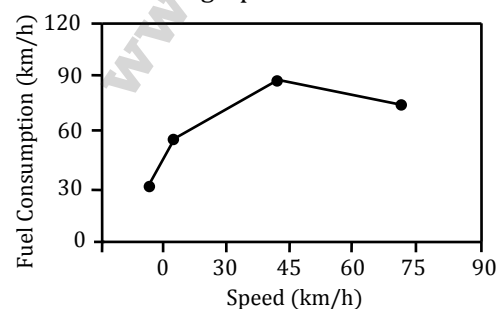62. The fuel consumed by a motorcycle during a journey while travelling at various speeds is indicated in the graph below.



The distances covered during four laps of the journey are listed in the table below

| Lap | Distance (kilometers) | Average Speed (km/h) |
|-----|-----------------------|----------------------|
| P | 15 | 15 |
| Q | 75 | 45 |
| R | 40 | 75 |
| S | 10 | 10 |

From the given data we can conclude that the fuel consumed per kilometer was least during the lap

- (A) P (C) R
(B) Q (D) S

[Ans. A]

63. Three friends, R, S and T shared toffee from a bowl. R took $\frac{1}{3}$ rd of the toffees, but returned four to the bowl. S took $\frac{1}{4}$ th of what was left but returned three toffees to the bowl. T took half of the remainder but returned two back into the bowl. If the bowl had 17 toffees left, how many toffees-were originally there in the bowl?

- (A) 38 (C) 48
(B) 31 (D) 41

[Ans. C]

64. Given that $f(y) = |y| / y$, and q is any non-zero real number, the value of $|f(q) - f(-q)|$ is

- (A) 0 (C) 1
(B) -1 (D) 2

[Ans. D]

65. The sum of n terms of the series $4 + 44 + 444 + \dots$ is

- (A) $\left(\frac{4}{81}\right) [10^{n+1} - 9n - 1]$
(B) $\left(\frac{4}{81}\right) [10^{n-1} - 9n - 1]$
(C) $\left(\frac{4}{81}\right) [10^{n+1} - 9n - 10]$
(D) $\left(\frac{4}{81}\right) [10^n - 9n - 10]$

[Ans. C]